

CIRCUIT THEORY (ECPC-101)
Date: 8 April 2025

MAX. MARKS: 15

Following information must be mentioned on the first page of the answer sheet


1. Section 2. Roll Number

3. Name of the student

4. Subject code

[8]

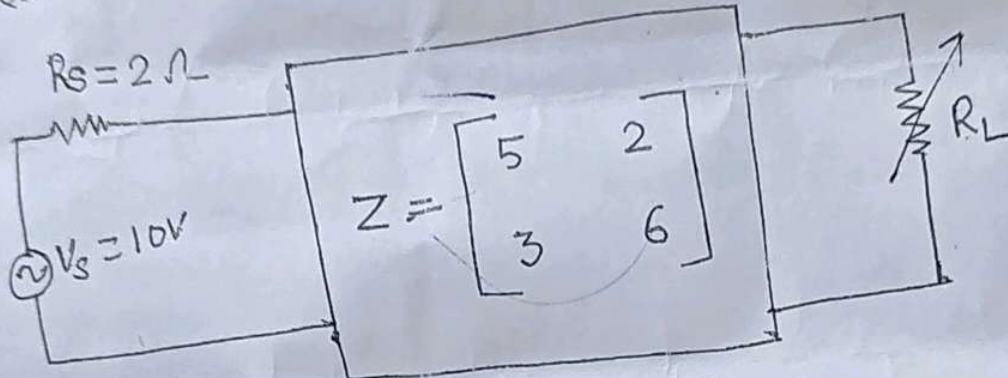Q1. Find maximum power dissipation in load resistor.



[Hint: Apply Thevenin's theorem]

Q2. Find $V(s)$ when $i_L(0) = 2A$ (initial current of inductor is 2A) and $V_c(0) = 3V$ (initial voltage of capacitor)

[7]

